



**Hack
and**

Slash

CPU Design

short presentation by: siavoosh payandeh azad

How long does it take?

- **To hack everything in, test each part and put them together you need 10-12 hours of coding...**
- **3 sessions is 12 hours...**

How long does it take?

- To hack everything in, test each part and put them together you need 10-12 hours of coding...
- 3 sessions is 12 hours...

so you should be fine...




Where to start?

- Well we have to **define the problem** first
- We have to **choose our approach** to solve it

State the problem

- **We want a CPU that does these things:**
 - **Addition/Subtraction**
 - **Increment/Decrement**
 - **Arithmetic and Logical Shift**
 - **Bitwise AND, OR and XOR**
 - **Negation**
 - **Load/Store**
 - **Unconditional Branch (jump)**
 - **Branch if zero / Branch if Overflow**
 - **Set/Clear Registers/Flags**
 - **NOP/HALT**

What are the parts?

 

What do we have?

- 8 bits Operands
- 16 Bits of Instruction (5 bit opcode = 32 different instructions)
- 1 Accumulator
- 1 general purpose register

What do we have?

- 8 bits Operands
- 16 Bits of Instruction (5 bit opcode = 32 different instructions)
- 1 Accumulator
- 1 general purpose register
- **No fancy stuff...**

INSTRUCTION SET

Instruction	Operand
Add_A_B	----
Add_A_Mem	Memory Address
Sub_A_B	----
Sub_A_Mem	Memory Address
IncA	----
DecA	----
ShiftA_R	----
ShiftA_L	----
And_A_B	----
OR_A_B	----
XOR_A_B;	----
NegA	----
Set/ Clear Z	----
Set/ Clear OV	----

INSTRUCTION SET

Instruction	Operand
Add_A_B	----
Add_A_Mem	Memory Address
Sub_A_B	----
Sub_A_Mem	Memory Address
IncA	----
DecA	----
ShiftA_R	----
ShiftA_L	----
And_A_B	----
OR_A_B	----
XOR_A_B;	----
NegA	----
Set/ Clear Z	----
Set/ Clear OV	----

Instruction	Operand
Load_Mem_B	Memory Address
Store_A_Mem	Memory Address

INSTRUCTION SET

Instruction	Operand
Add_A_B	----
Add_A_Mem	Memory Address
Sub_A_B	----
Sub_A_Mem	Memory Address
IncA	----
DecA	----
ShiftA_R	----
ShiftA_L	----
And_A_B	----
OR_A_B	----
XOR_A_B;	----
NegA	----
Set/ Clear Z	----
Set/ Clear OV	----

Instruction	Operand
Load_Mem_B	Memory Address
Store_A_Mem	Memory Address

Instruction	Operand
Jmp	Inst memory Address
Jmp_OV	Inst memory Address
Jmp_Z	Inst memory Address

INSTRUCTION SET

Instruction	Operand
Add_A_B	----
Add_A_Mem	Memory Address
Sub_A_B	----
Sub_A_Mem	Memory Address
IncA	----
DecA	----
ShiftA_R	----
ShiftA_L	----
And_A_B	----
OR_A_B	----
XOR_A_B;	----
NegA	----
Set/ Clear Z	----
Set/ Clear OV	----

Instruction	Operand
Load_Mem_B	Memory Address
Store_A_Mem	Memory Address

Instruction	Operand
Jmp	Inst memory Address
Jmp_OV	Inst memory Address
Jmp_Z	Inst memory Address

Instruction	Operand
NOP	-----
HALT	-----

INSTRUCTION SET

Instruction	Operand
Add_A_B	----
Add_A_Mem	Memory Address
Sub_A_B	----
Sub_A_Mem	Memory Address
IncA	
DecA	
ShiftA_R	
ShiftA_L	
And_A_B	
OR_A_B	
XOR_A_B;	----
NegA	----
Set/ Clear Z	----
Set/ Clear OV	----

Instruction	Operand
Load_Mem_B	Memory Address
Store_A_Mem	Memory Address


21 Instructions

NOP	----
HALT	----


INSTRUCTION SET




Starting from DPU

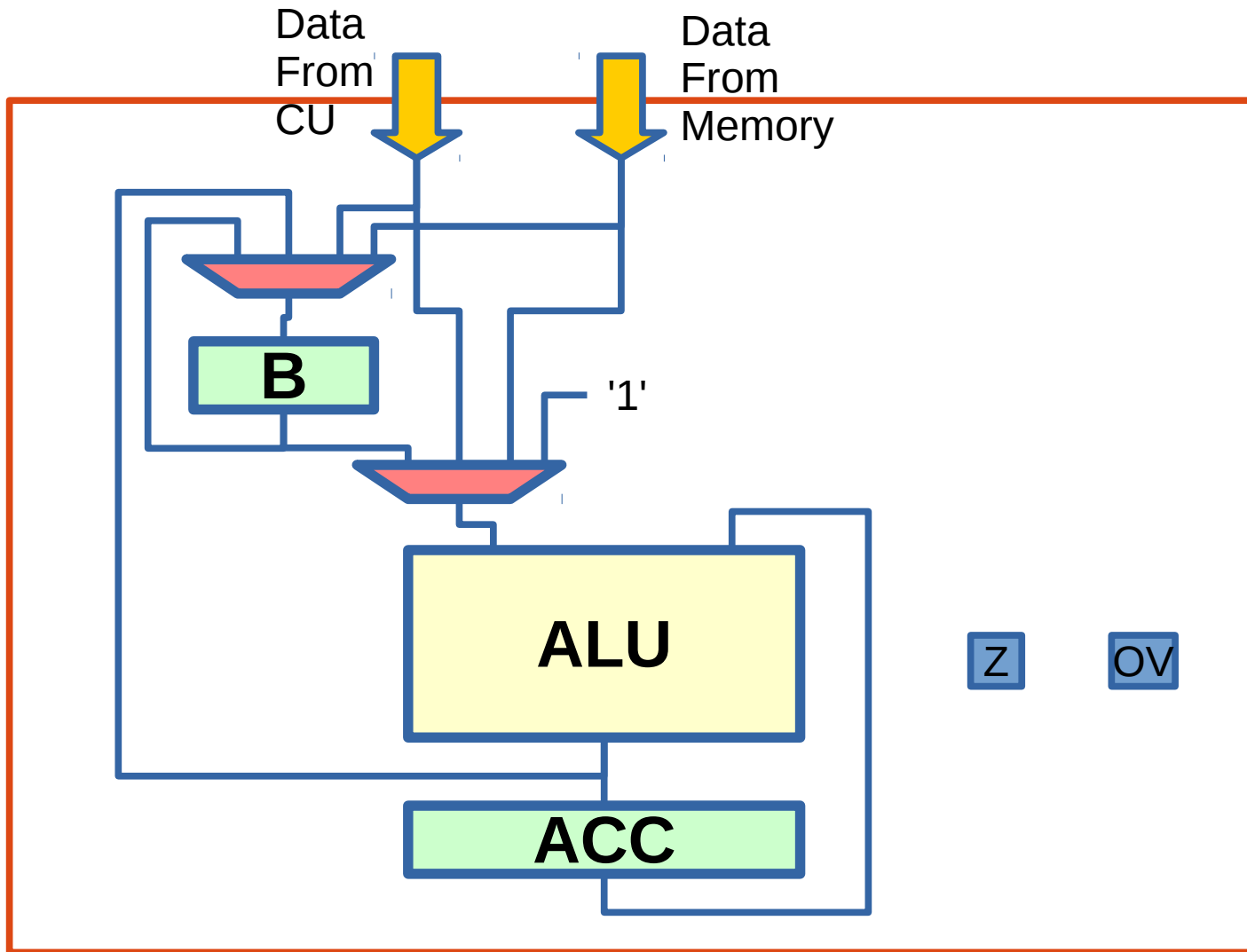


Starting from DPU

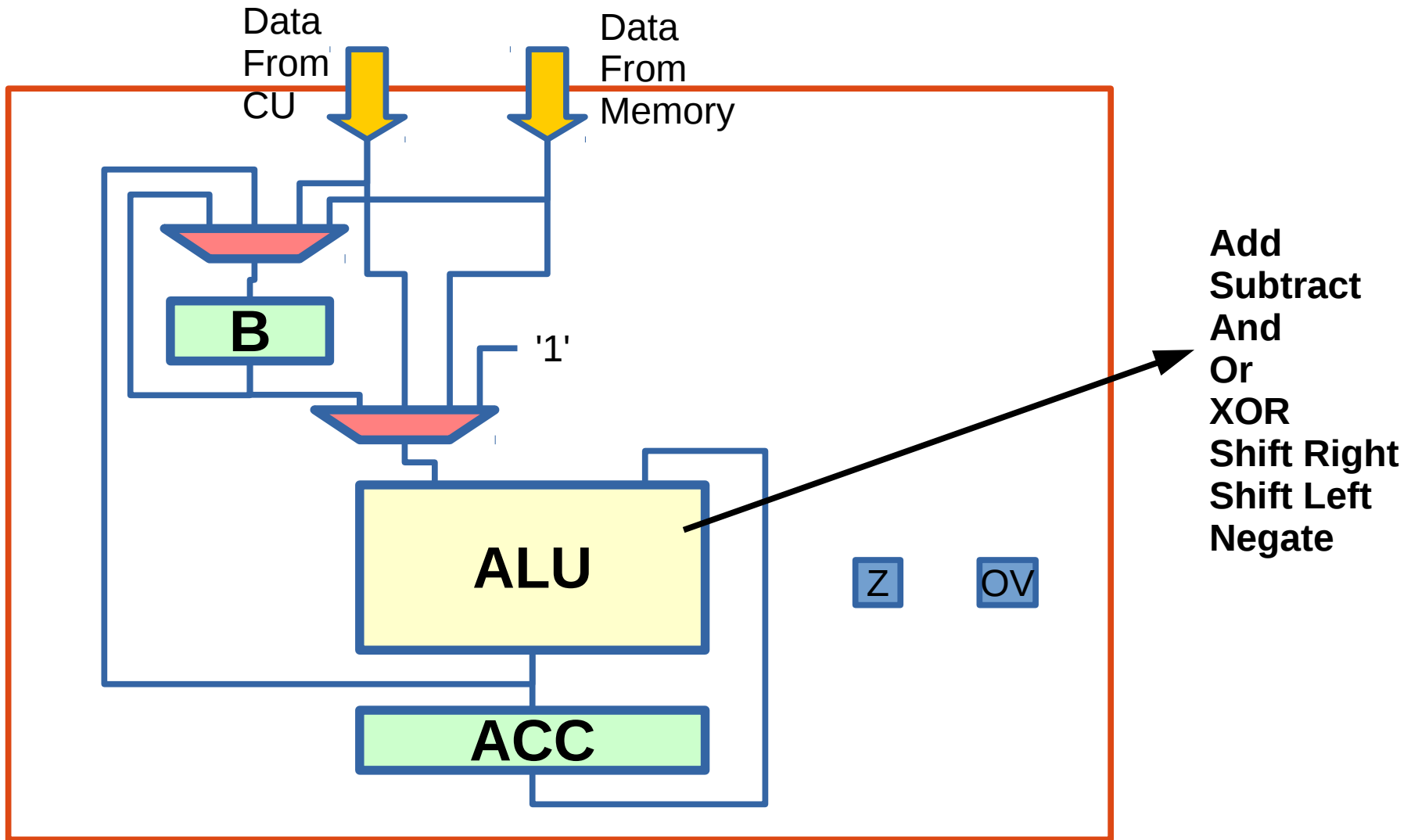

Starting from DPU

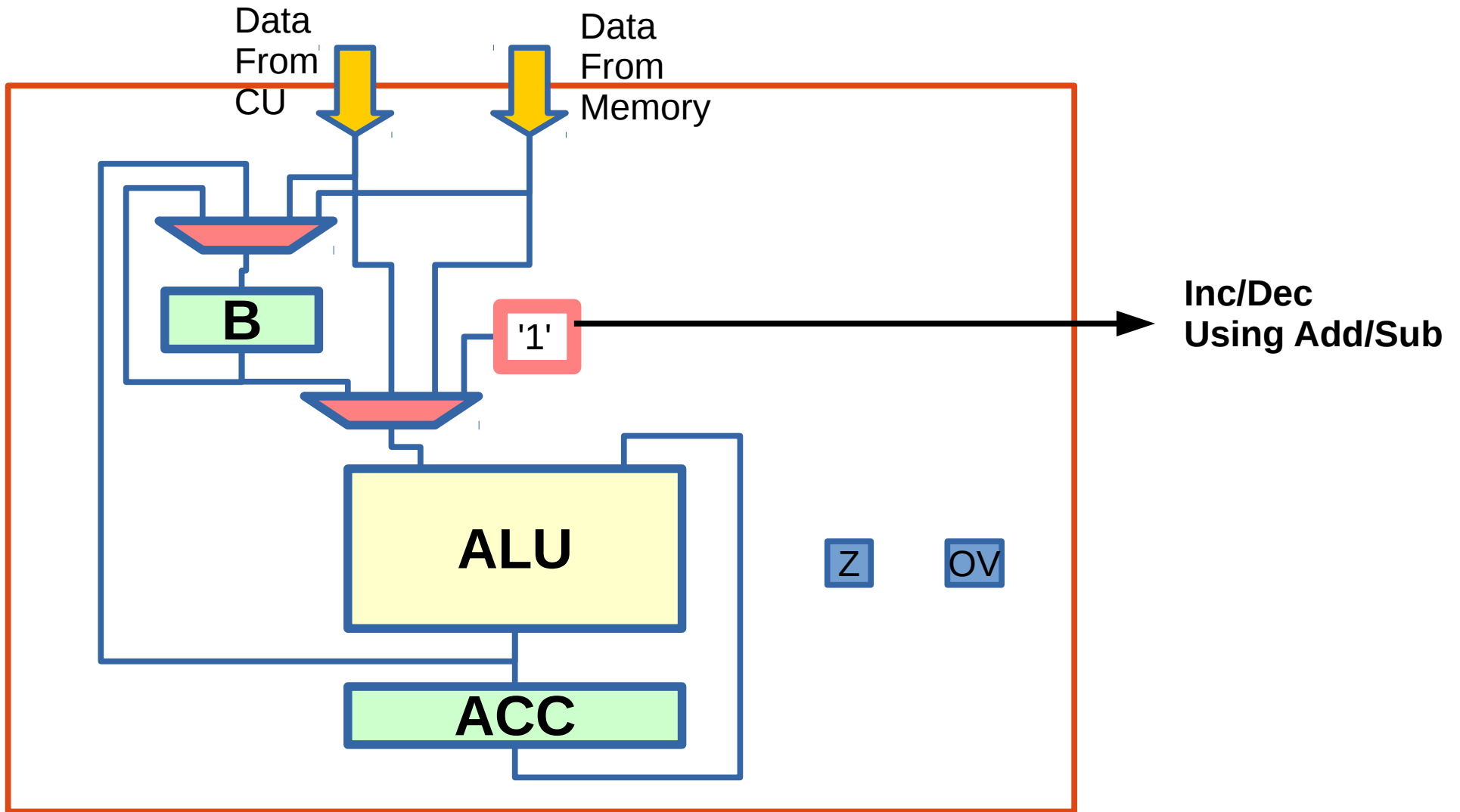

Starting from DPU

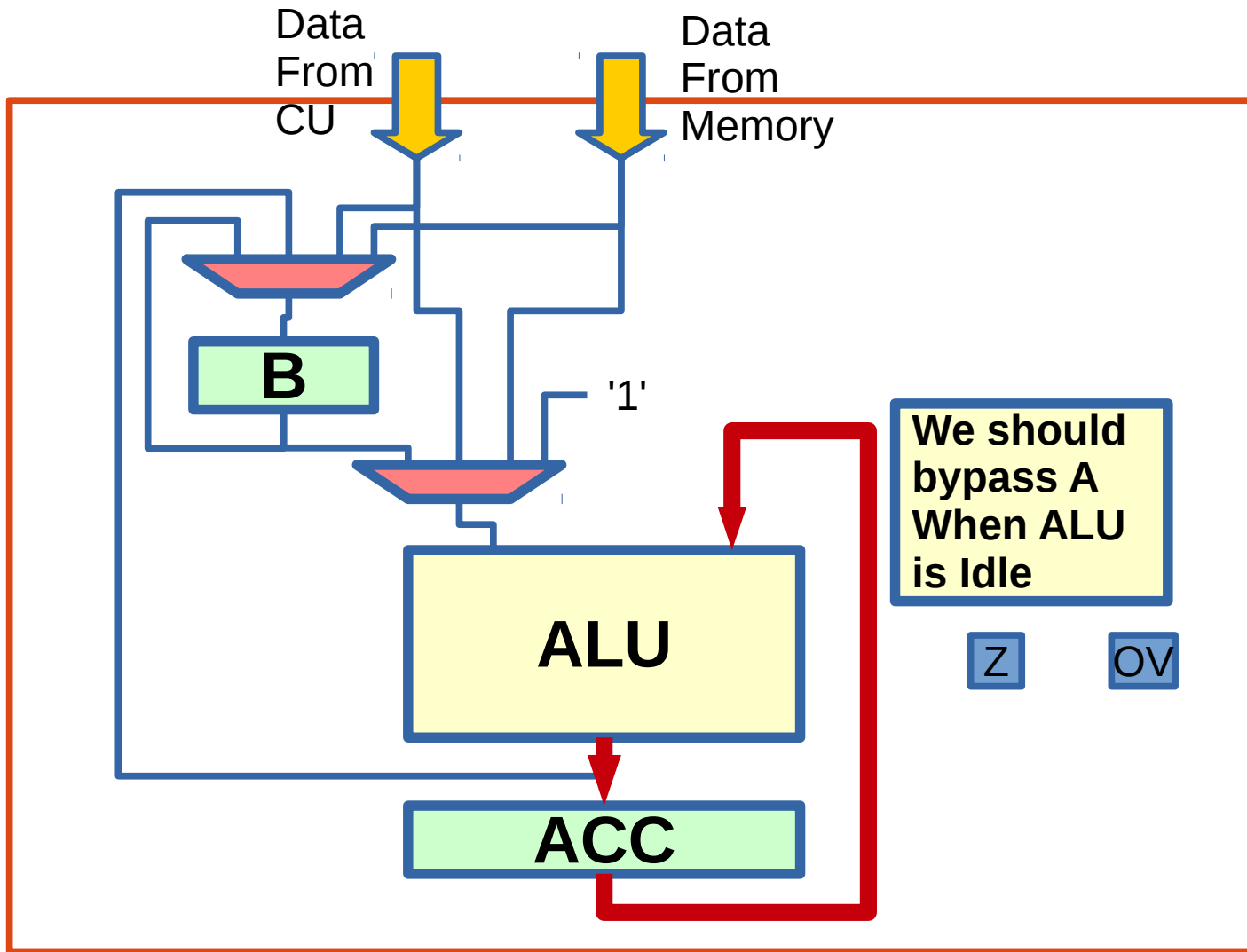

Lets break the ALU


```
PROC_ALU: process(Command,A,B)
begin

  case Command is
    WHEN some condition => --add
    WHEN some condition => -- Subtract
                          --Bypass A
                          --Bypass B
    ....
                          --And
                          --or
                          --xor
                          --shift right
                          --shift left
    WHEN some condition => --negation

    WHEN OTHERS => Result <= "00000000";
  END CASE;

end process PROC_ALU;
```


Starting from DPU

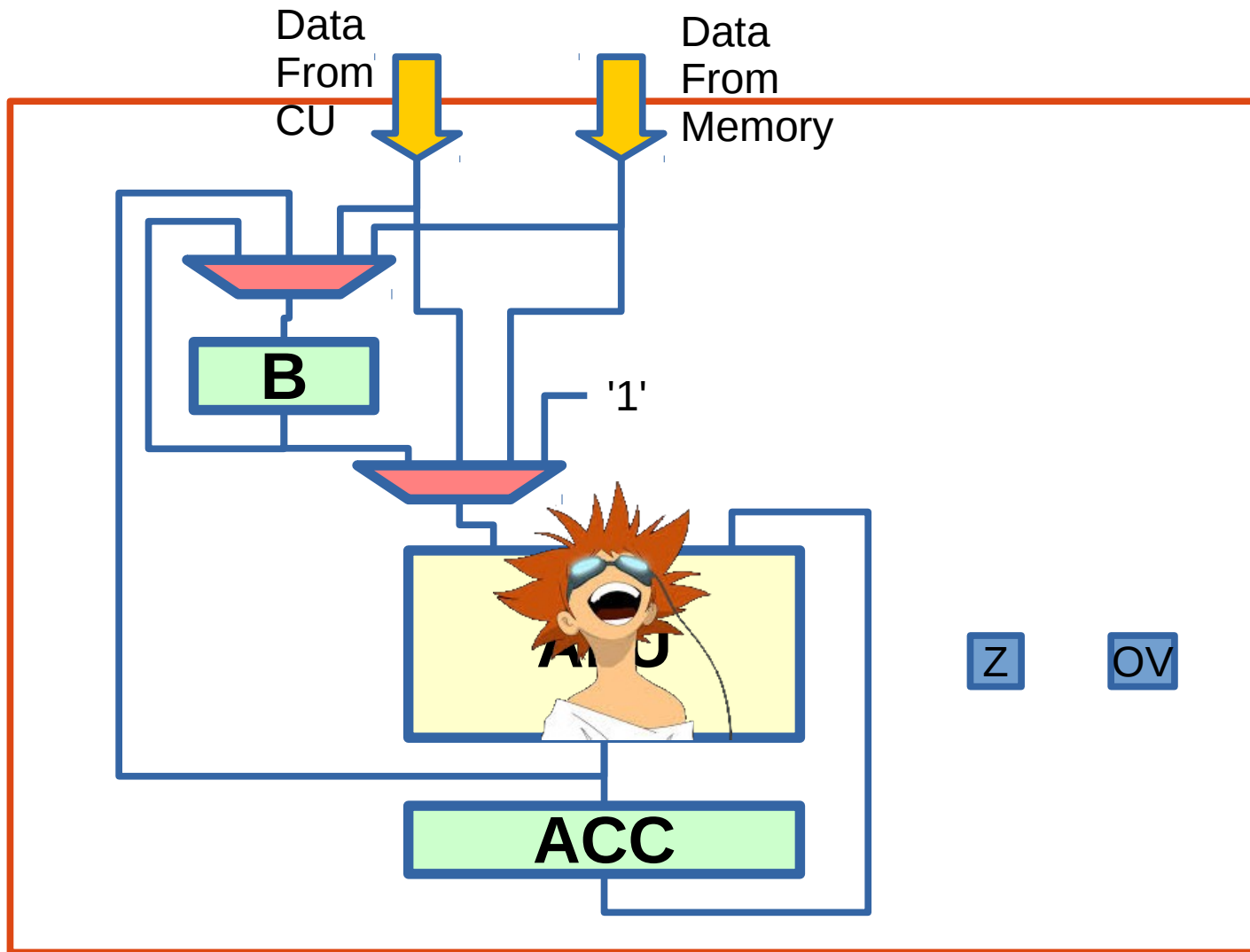

Multiplexers


```
process
(Data_in_mem,Data_in,B_out,Mux_Cont)
begin
  case Mux_Cont is
    When "00" => .....
    when "01" => .....
    when "10" => .....
    when "11" => .....
    when others => .....
  end case;
end process;
```

Starting from DPU

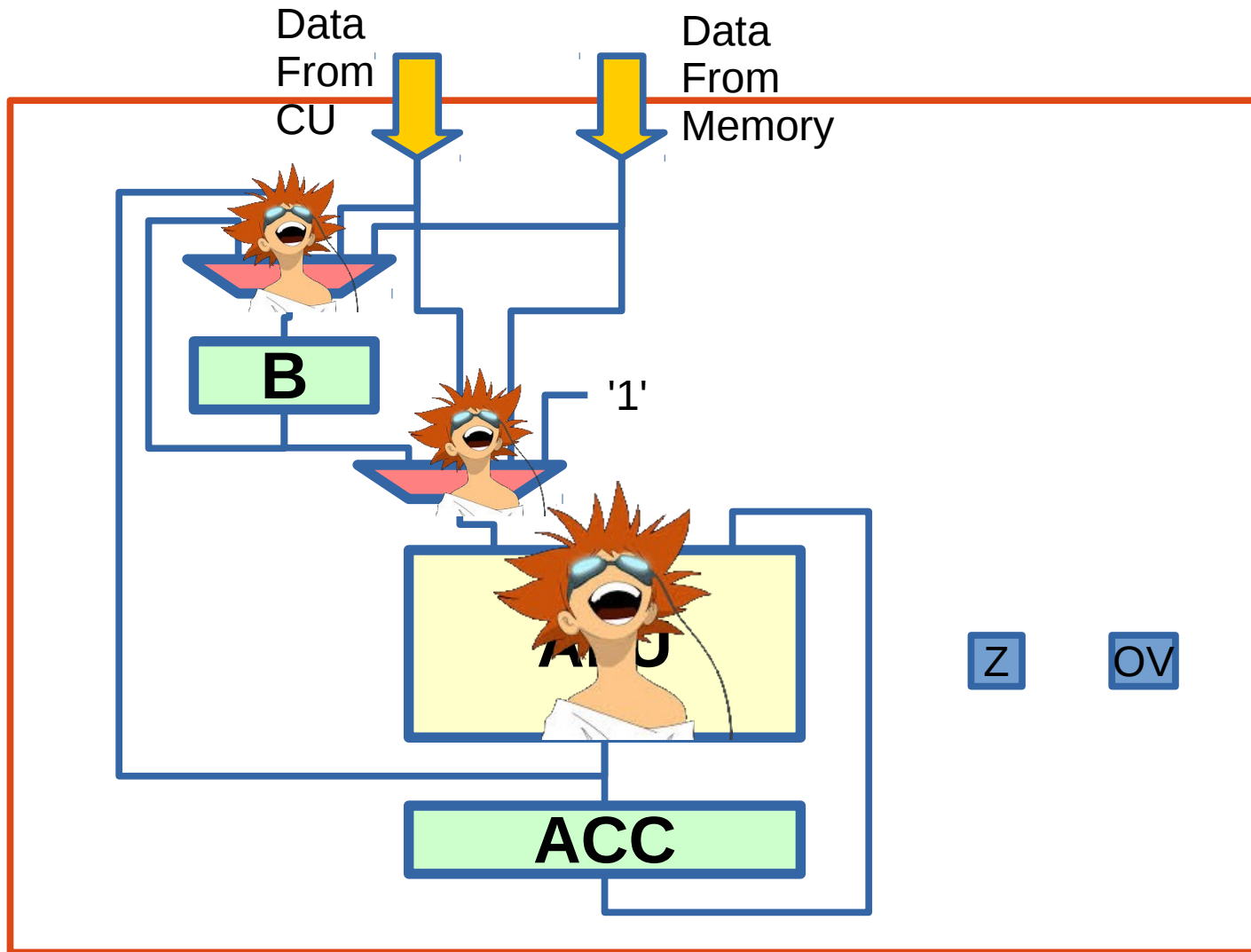


Flags
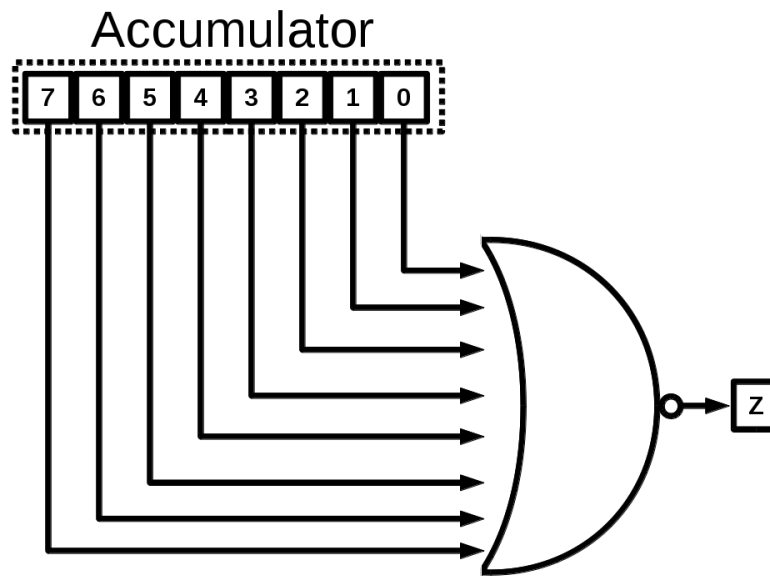
$$OV = (A[8] \cdot B[8] \cdot \overline{R[8]}) \mid (\overline{A[8]} \cdot \overline{B[8]} \cdot R[8])$$




Starting from DPU

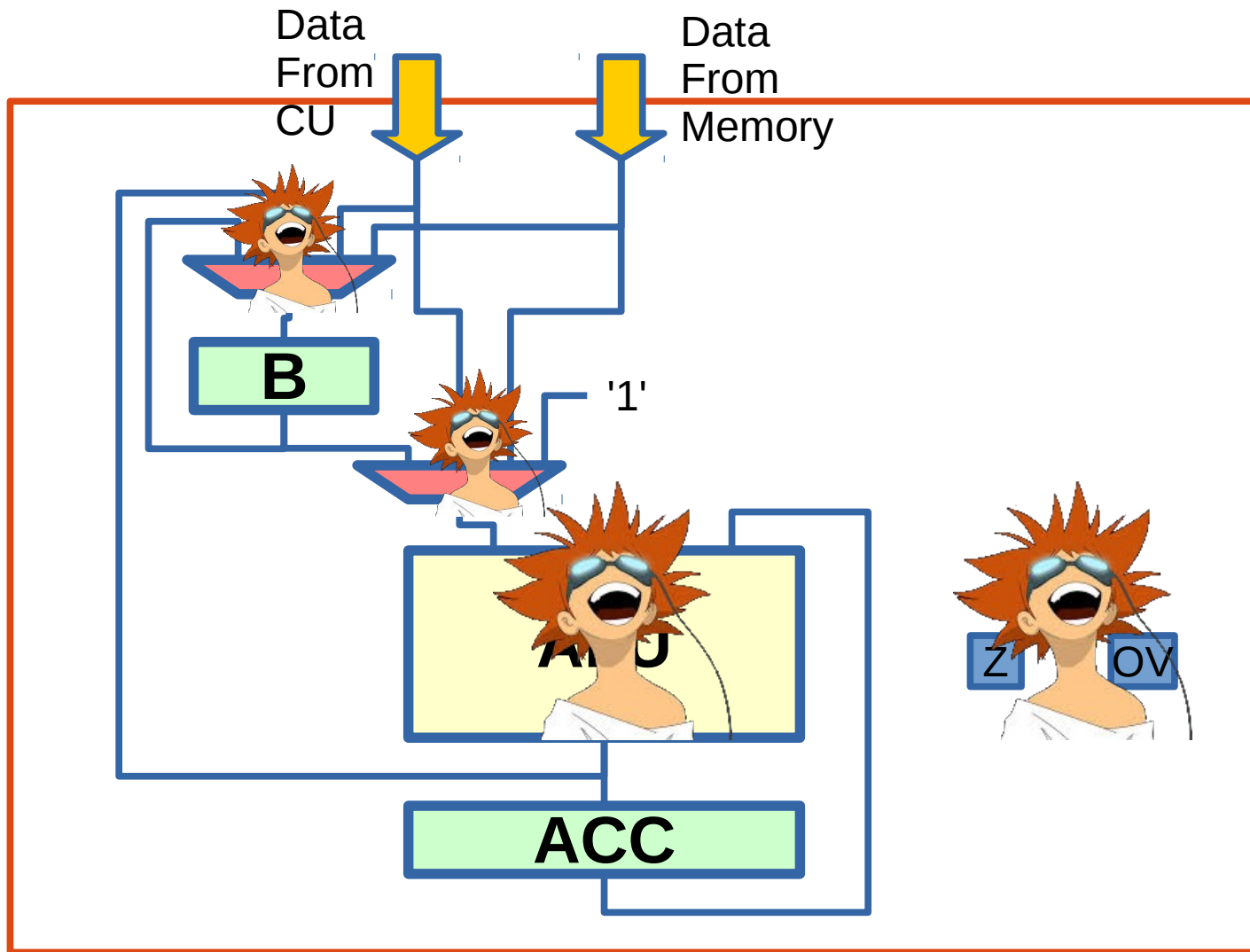

Test

it...

DATA Memory

 

architecture beh of Mem is

```
type Mem_type is array (0 to 255) of std_logic_vector(7 downto 0);  
signal Mem : Mem_type;
```

```
begin
```

```
MemProcess: process(clk,rst) is
```

```
begin
```

```
    if rst = '1' then
```

```
        Mem <= ((others=> (others=>'0')));
```

```
    elsif rising_edge(clk) then
```

```
        if RW = '1' then
```

```
            Mem(to_integer(unsigned(Address))) <= Data_in;
```

```
        end if;
```

```
    end if;
```

```
end process MemProcess;
```

```
Data_Out <= Mem(to_integer(unsigned(Address)));
```

```
end beh;
```

architecture beh of Mem is

```
type Mem  
signal Me
```

```
(7 downto 0);
```

Piece of cake

```
begin  
MemProces  
begin
```


```
if rst = '1'  
Mem <= ((others=> (others=> 0))),  
elsif rising_edge(clk) then  
if RW = '1' then
```

```
Mem(to_integer(unsigned(Address))) <= Data_
```

```
end if;  
end if;  
end process MemProcess;
```

```
Data_Out <= Mem(to_integer(unsigned(Address)))
```


```
end beh;
```

 

Test

it...

Instruction Memory

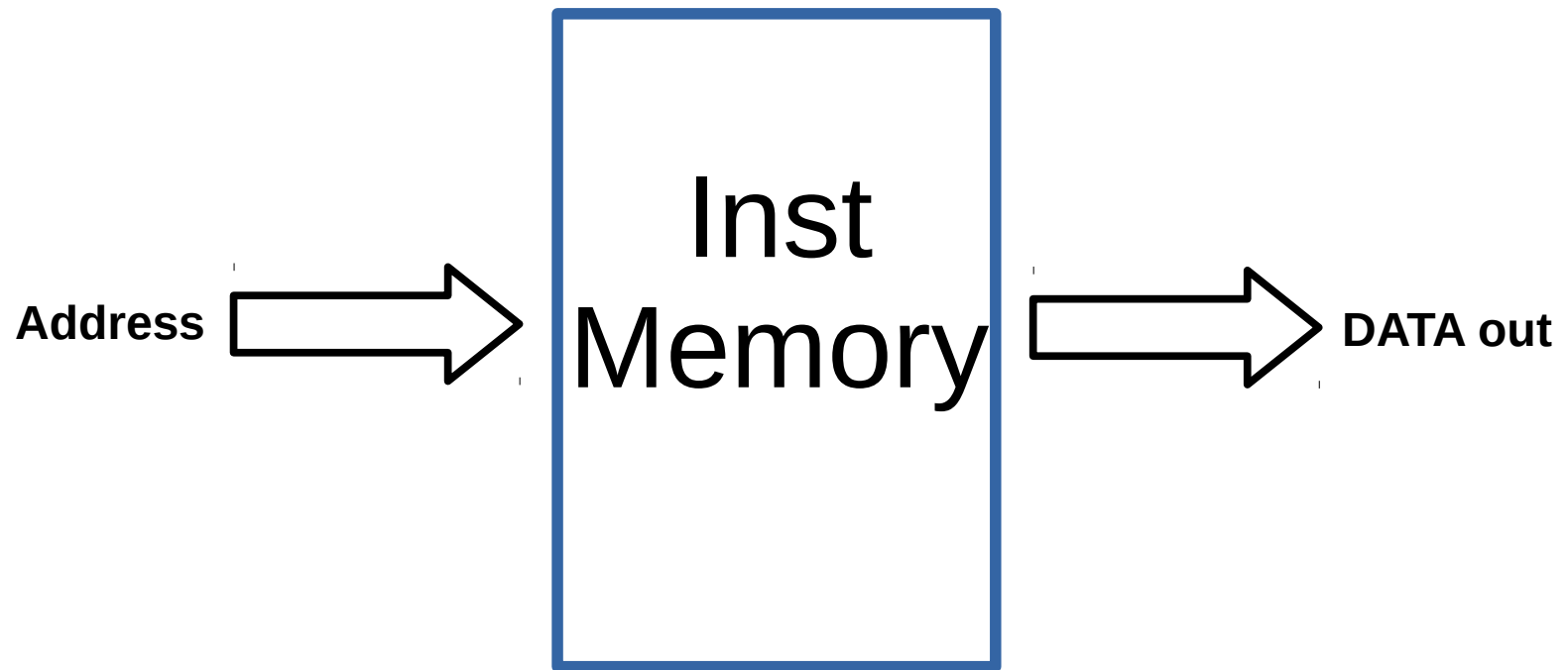

```
entity InstMem is
  port ( address : in std_logic_vector(7 downto 0);
        data : out std_logic_vector(15 downto 0) );
end entity InstMem;
```

architecture behavioral of InstMem is

```
type mem is array ( 0 to 255) of std_logic_vector(15 downto 0);
  constant my_InstMem : mem := (
    0 => instr 0
    1 => instr 1
    2 => instr 2
    .....
    254 => instr 254
    255 => Halt
  );
```

begin

```
data <= my_InstMem(to_integer(unsigned(address)));
end architecture behavioral;
```

```
entity InstMem is
  port ( address : in std_logic_vector(15 downto 0);
        data : out std_logic_vector(15 downto 0);
end entity InstMem
```

```
architecture behavioral of InstMem
```

```
  type mem_type is array(0 to 15) of std_logic_vector(15 downto 0);
  constant mem : mem_type := (15 downto 0) => (15 downto 0) =>
```

```
);
```

```
begin
```


```
  data <= my_InstMem(to_integer(unsigned(address)));
end architecture behavioral;
```




Test

it...


Control Unit

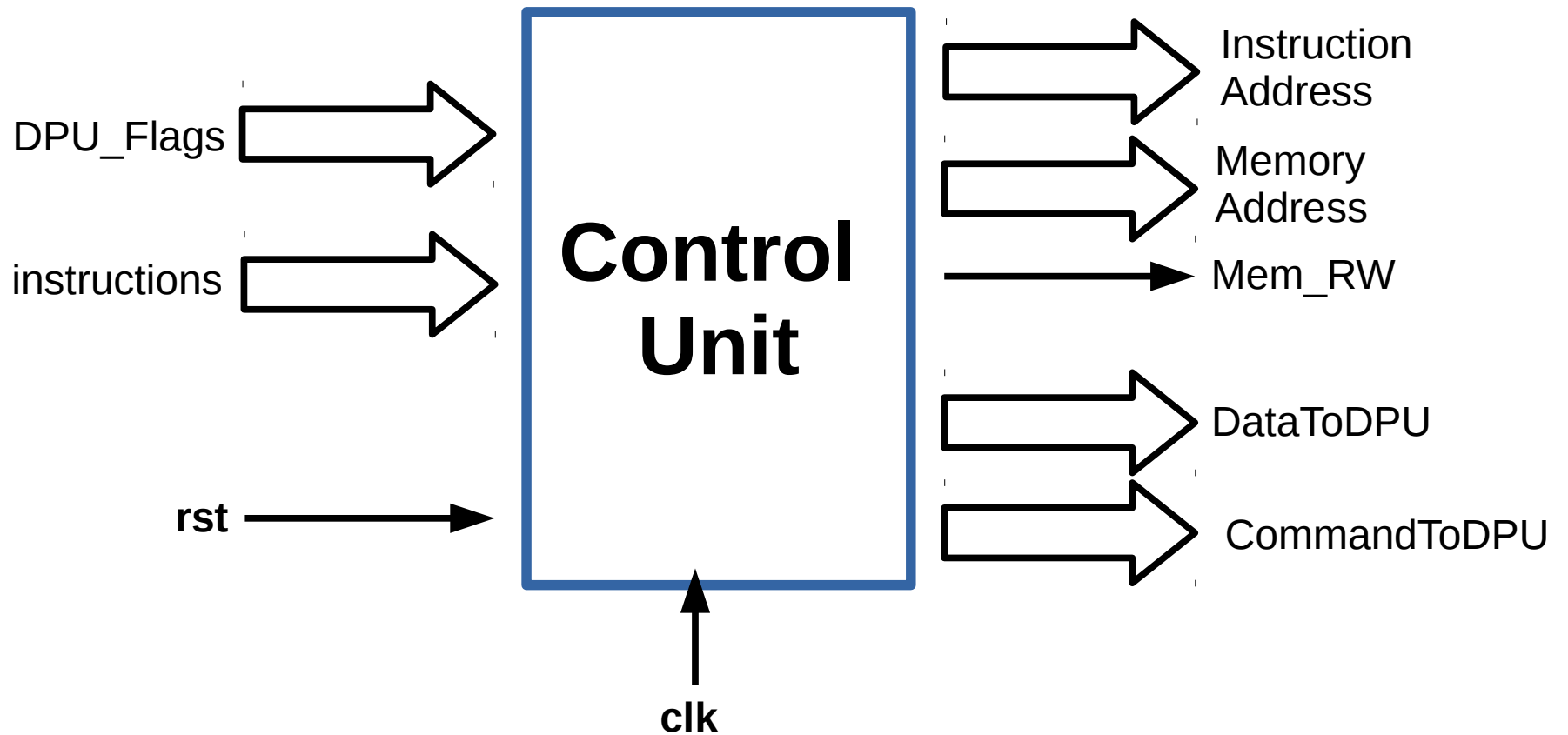

Block diagram

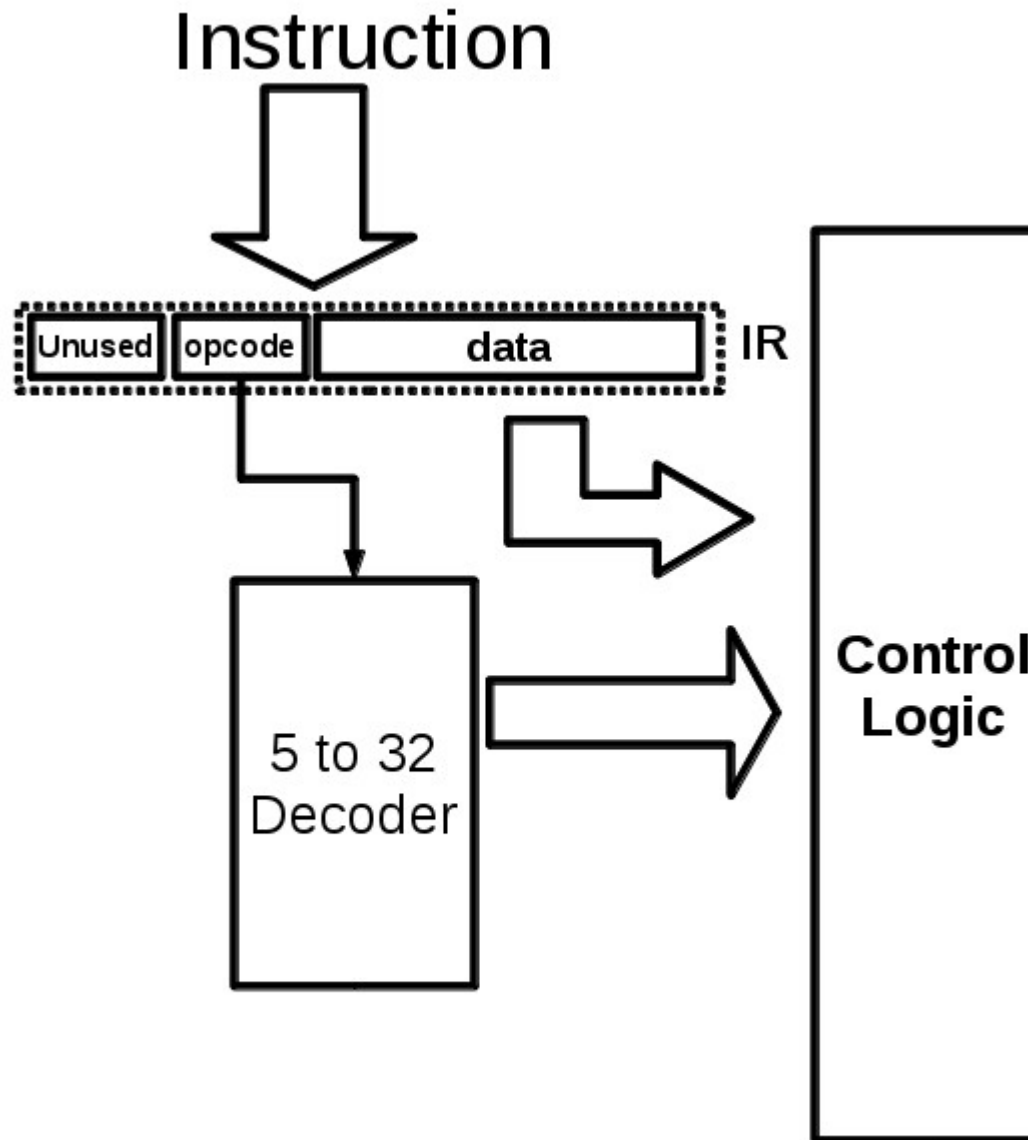

THE FSM

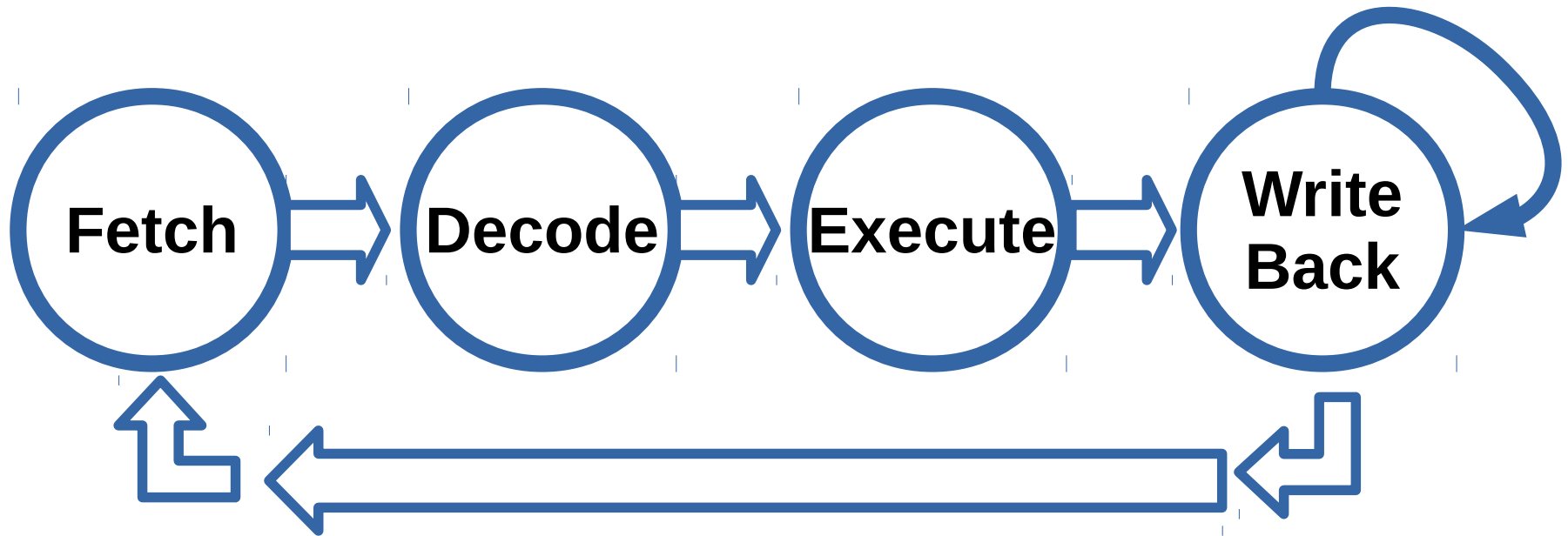

```
TYPE STATE_TYPE IS (Fetch, Decode, Execution,WriteBack);  
Signal State_in, State_out :STATE_TYPE;
```

```
CASE State_out IS  
    WHEN Fetch =>  
        State_in <= Decode;  
    WHEN Decode =>  
        State_in <= Execution;  
    WHEN Execution =>  
        State_in <= WriteBack;  
    WHEN WriteBack =>  
        if Instr = HALT then  
            State_in <= WriteBack;  
        Else  
            State_in <= Fetch;  
        end if;  
END case;
```

Make Registers

```
-----  
process (clk,rst)  
begin  
  if rst = '1' then  
  
    State_out <= Fetch;  
    PC_out <= "00000000";  
    InstrReg_out <= (others => '0');  
  
  elsif clk'event and clk='1' then  
  
    State_out <= State_in;  
    PC_out <= PC_in;  
    InstrReg_out <= InstrReg_in;  
  
  end if;  
end process;  
-----
```

Fetch

```
WHEN Fetch =>  
    DataToDPU <= "00000000";  
    MemAddress <= "00000000";  
    CommandToDPU <= --stay idle  
    Instr_Add <= PC_out;  
    Mem_RW <= '0';  
    State_in <= Decode;
```

Decode

```
WHEN Decode =>  
  DataToDPU <= "00000000";  
  MemAddress <= "00000000";  
  CommandToDPU <= --do not do anything  
  State_in <= Execution;
```

Wait for instruction
decoder to finish



Decoder...

```
TYPE Instruction IS ( Add_A_B,  
Add_A_Mem, Sub_A_B, Sub_A_Mem,  
IncA, DecA, ShiftA_R, ShiftA_L, And_A_B,  
OR_A_B, XOR_A_B, Load_Mem_B,  
LoadBControl, Store_A_Mem, Jmp, JmpZ,  
JmpOV, SetZ, ClearZ, SetOV, ClearOV,  
NOP, HALT, NegA);
```

```
Signal Instr:Instruction;
```

```
process (opcode) -- Instr decoder  
begin  
  case opcode is  
    when "00000" => Instr <= Add_A_B;  
    when "00001" => Instr <= Add_A_Mem;  
    when "00010" => Instr <= Sub_A_B;  
    when "00011" => Instr <= Sub_A_Mem;  
    when "00100" => Instr <= IncA;  
    when "00101" => Instr <= DecA;  
  
    .....  
    when "11000" => Instr <= NOP;  
    when "11001" => Instr <= HALT;  
    when "11010" => Instr <= NegA;  
    when "11011" => Instr <= LoadBControl;  
    when others => Instr <= NOP;  
  end case;  
end process;
```



Off with their heads (Execute)

```
WHEN Execution =>
```

```
  DataToDPU <= "00000000";
```

```
  MemAddress <= "00000000";
```

```
  Mem_RW <= '0';
```

```
  if Instr = Add_A_B then
```

```
    CommandToDPU <= -- Add command
```

```
  elsif Instr = Add_A_Mem then
```

```
    MemAddress <= -- proper memory address
```

```
    CommandToDPU <= -- memory load command
```

```
    .....
```

```
  elsif Instr = HALT then
```

```
    CommandToDPU <= --Stay Idle
```

```
  else
```

```
    CommandToDPU <= --Stay Idle
```

```
  end if;
```

```
  State_in <= WriteBack;
```

Write Back

WHEN **WriteBack** =>

```
DataToDPU <= "00000000";  
MemAddress <= "00000000";  
CommandToDPU <= --Stay Idle
```

```
if Instr = Store_A_Mem then
```

```
    MemAddress <= – proper memory address
```

```
    Mem_RW <= '1';
```

```
    PC_in <= PC_out+1;
```

```
    State_in <= Fetch;
```

```
elseif Instr = HALT then
```

```
    PC_in <= PC_out;
```

```
    State_in <= WriteBack;
```

```
elseif Instr = Jmp then
```

```
    PC_in <= – proper memory address
```

```
    State_in <= Fetch;
```

```
elseif Instr = JmpZ and DPU_Flags(2) = '1' then
```

```
    PC_in <= – proper memory address
```

```
    State_in <= Fetch;
```

```
elseif Instr = JmpOV and DPU_Flags(0) = '1' then
```

```
    PC_in <= – proper memory address
```

```
    State_in <= Fetch;
```

```
else
```

```
    PC_in <= PC_out+1;
```

```
    State_in <= Fetch;
```


```
end if;
```



Test

it...

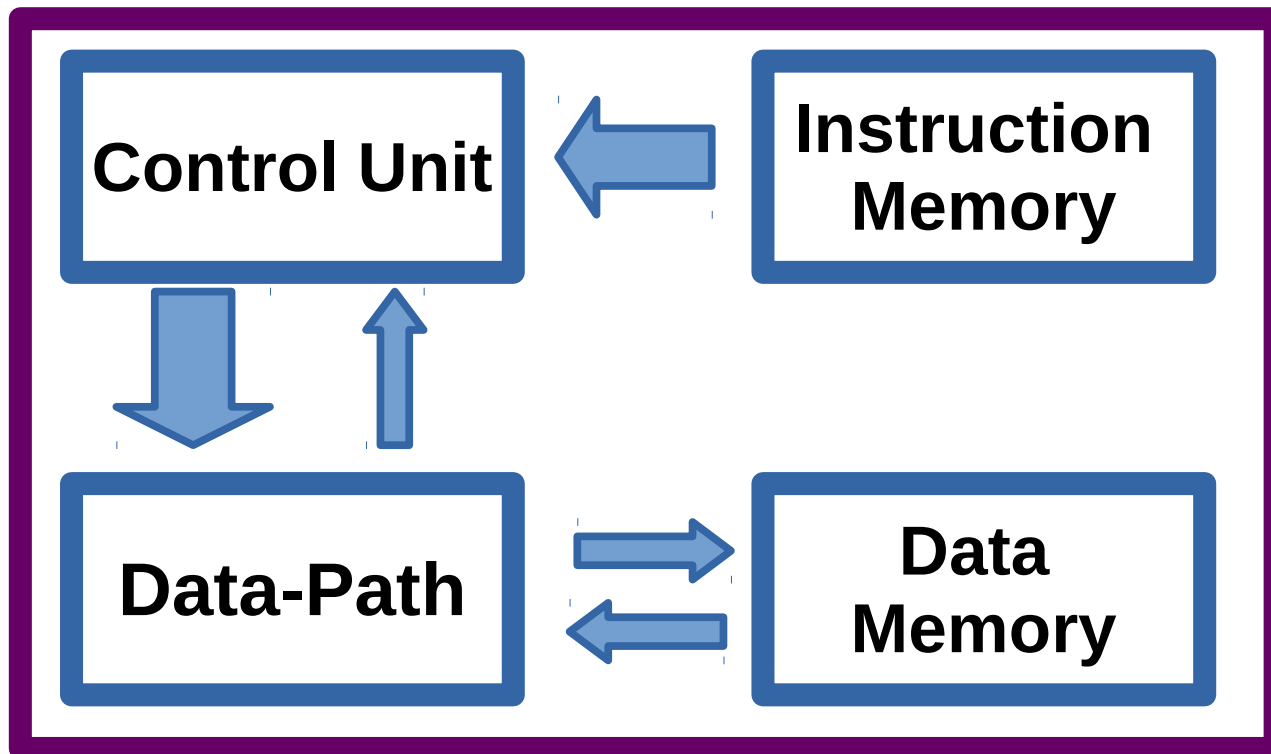Now... lets put everything back together...



And
Hacking
Begins...

